


Experiment #3 - Function Generator

Ali_imangholi

810197692

ali.imangholi@ut.ac.ir

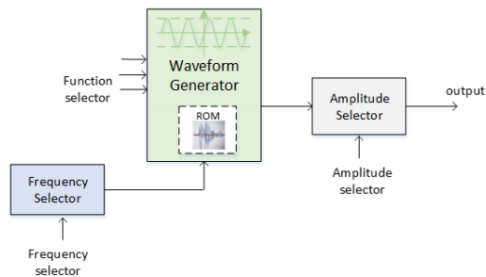Abstract— In this lab we want to design a function generator for this goal we use clock divider of lab 1 To make clk a control frequency of signals For design the function generator we use 3 part:



INTRODUCTION

We want make the signal that list below:

| func [2:0] | Function |
|------------|-----------------------|
| 3'b000 | Rhomboid |
| 3'b001 | Sine |
| 3'b010 | Square |
| 3'b011 | Reciprocal |
| 3'b100 | Saw-tooth |
| 3'b101 | Full-wave rectified |
| 3'b110 | Modulated square wave |
| 3'b111 | Arbitrary |


Waveform Generator

In this part we write a Verilog codes for generating signals:
This pictures are the simulation result:


Rhomboid:




Sine:

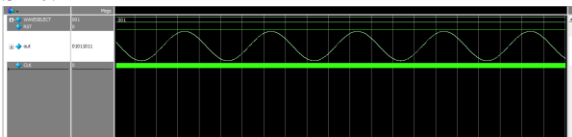


Square:

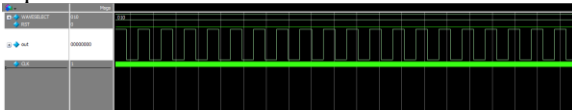


Reciprocal:

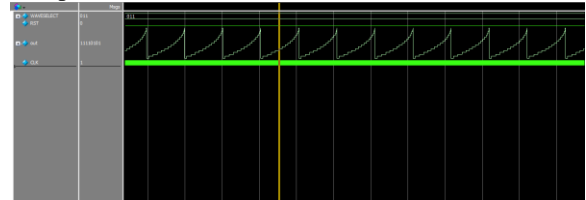

Saw_tooth:

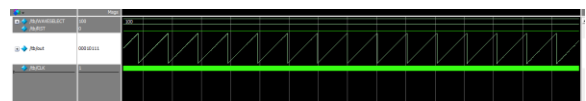

Full-Wave rectified:

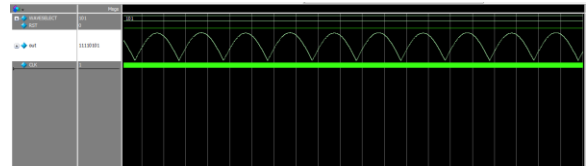


Modulated square Wave:




Arbitrary:

Use Quartus synthesis:

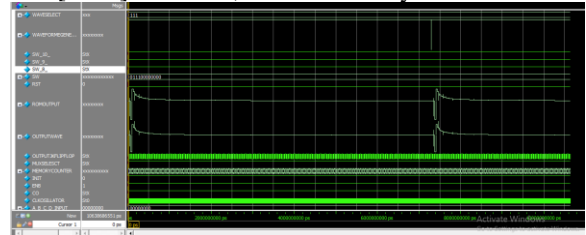SW [10..8] = 3'b111; chose Arbitrary WaveForm.




SW [10..8] = 3'b001 chose Sine WaveForm.

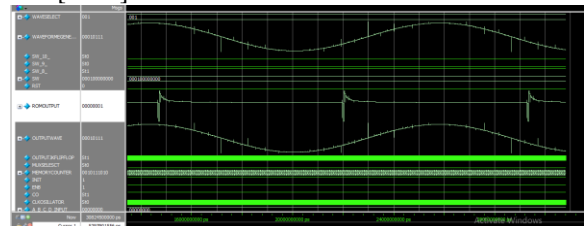


Frequency Selector


SW[7..0]=8'b00000010;

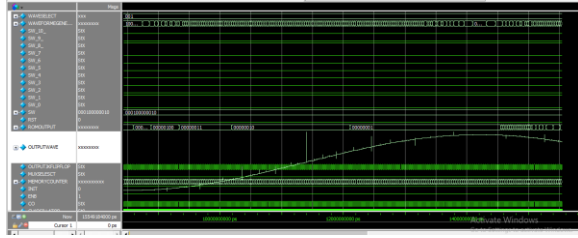


SW[7..0]=8'b00000100;

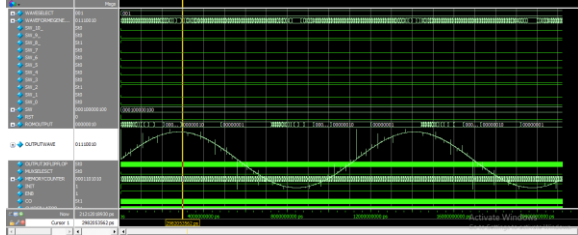


SW[7..0]=8'b00111000;

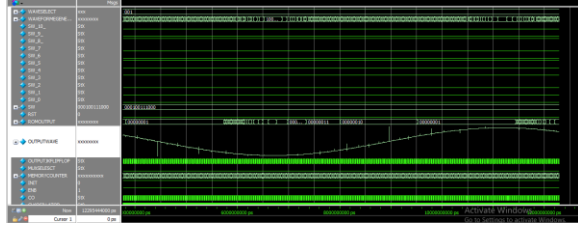

SW[7..0]=8'b10000000;

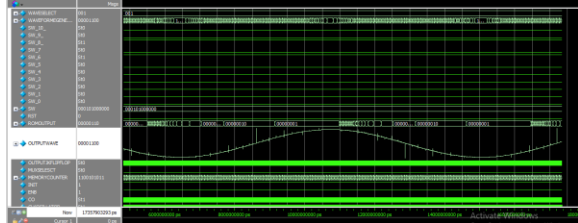

SW[7..0]=8'b11111111;

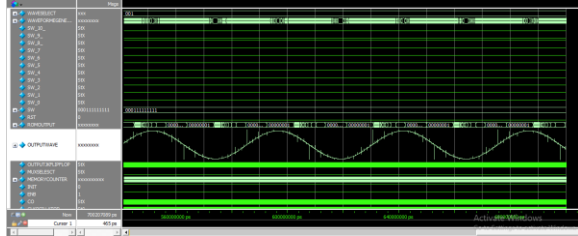


Amplitude Selector


Table 2: Amplitude selection

| SW[12:11] | Amplitude |
|-----------|-----------|
| 2'b00 | 1 |
| 2'b01 | 2 |
| 2'b10 | 4 |
| 2'b11 | 8 |


SW[12..11] = 2'b 00;

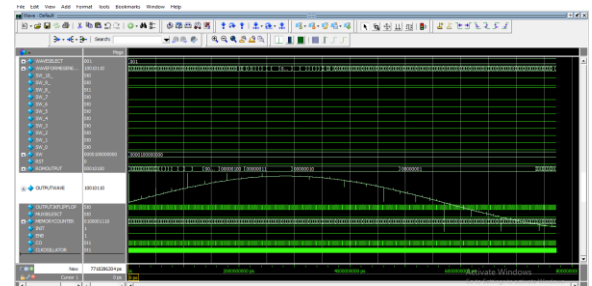


SW[12..11] = 2'b 01;

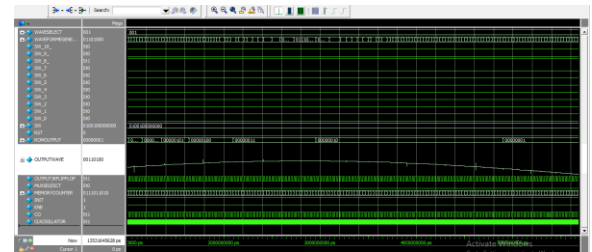


SW[12..11] = 2'b 10;

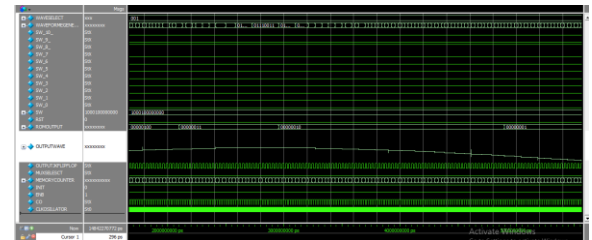

SW[12..11] = 2'b 11;

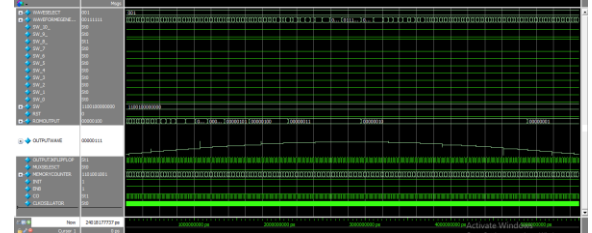

Final Quartus file:

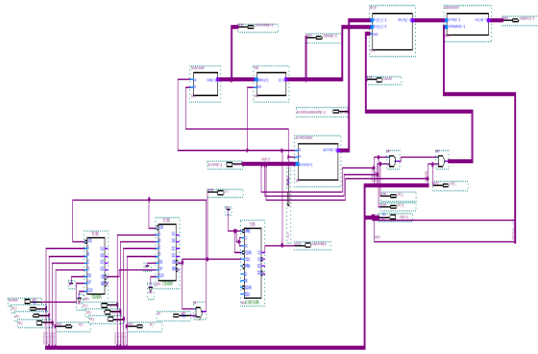

CONCLUSIONS

We conclude that we can made a function generator that have several waveform and we can select frequency and amplitude of this waveform.